



# Discussion 6

# Digital Circuit




Lehan Liu  
<liuh2024@>  
4/10/2026

# Overview




$$i\hbar \frac{\partial}{\partial t} |\psi(t)\rangle = \hat{H} |\psi(t)\rangle$$

semiconductor physics

 

semiconductor device

 

Included in CS110!



Circuits and Systems

Datapath

Machine code / ISA

# Logic



- Learn Laws of Boolean Algebra
- Be able to write the truth table
- Be able to simplify Boolean expression (by Karnaugh map or laws)
- Be able to convert the expression into certain form (or with certain gates)



# Laws of Boolean Algebra

AND form

OR form

$$X\bar{X} = 0$$

$$X+\bar{X} = 1$$

$$X0 = 0$$

$$X+1 = 1$$

$$X1 = X$$

$$X+0 = X$$

$$XX = X$$

$$X+X = X$$

$$XY = YX$$

$$X+Y = Y+X$$

$$(XY)Z = X(YZ)$$

$$(X+Y)+Z = X+(Y+Z)$$

$$X(Y+Z) = XY+XZ$$

$$X+YZ = (X+Y)(X+Z)$$

$$XY+X = X$$

$$(X+Y)X = X$$

$$\overline{XY} = \bar{X}+\bar{Y}$$

$$\overline{X+Y} = \bar{X}\bar{Y}$$

Complementarity

Laws of 0's and 1's

Identities

Idempotent Laws

Commutativity

Associativity

Distribution


Absorption

DeMorgan's Law

# Example



Logic abstraction

 

$R$	$A$	$G$	$Z$
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

# Example



- Get the Boolean expression


$$Z = R'A'G' + R'AG + RA'G + RAG' + RAG$$

- Simplify the Boolean expression

$$Z = R'A'G' + RA + RG + AG$$

How about the Karnaugh map?

- Draw the circuit

 



# Rules of Boolean Algebra

Basic rules of Boolean algebra.

---

1.  $A + 0 = A$

2.  $A + 1 = 1$

3.  $A \cdot 0 = 0$

4.  $A \cdot 1 = A$

5.  $A + A = A$

6.  $A + \bar{A} = 1$

7.  $A \cdot A = A$

8.  $A \cdot \bar{A} = 0$

9.  $\bar{\bar{A}} = A$

10.  $A + AB = A$

11.  $A + \bar{A}B = A + B$  \*

12.  $(A + B)(A + C) = A + BC$  \*

---

$A$ ,  $B$ , or  $C$  can represent a single variable or a combination of variables.

Proof:


$$AB + A'C + BC = AB + A'C$$

Proof:

$$AB + A'C + BCD = AB + A'C$$
 
# Rules of Boolean Algebra

- Rule 1:  $A + 0 = A$ , A variable ORed with 0 is always equal to the variable



- Rule 2:  $A + 1 = 1$ , A variable ORed with 1 is always equal to 1.



- Rule 3:  $A \cdot 0 = 0$ , A variable ANDed with 0 is always equal to 0.





- Rule 4:  $A \cdot 1 = A$ , A variable ANDed with 1 is always equal to the variable.




  
# Rules of Boolean Algebra

- Rule 5:  $A + A = A$ , A variable ORed with itself is always equal to the variable.



  - Rule 6:  $A + \bar{A} = 1$ , A variable ORed with its complement is always equal to 1.



- Rule 7:  $A \cdot A = A$ , A variable ANDed with itself is always equal to the variable.



- Rule 8:  $A \cdot \bar{A} = 0$ , A variable ANDed with its complement is always equal to 0.



# Rules of Boolean Algebra

- Rule 9: The double complement of a variable is always equal to the variable.



- Rule 10:  $A + AB = A$

$$\begin{aligned} A + AB &= A \cdot 1 + AB = A(1 + B) \\ &= A \cdot 1 \\ &= A \end{aligned}$$



# Rules of Boolean Algebra



- Rule 11:  $A + A'B = A + B$


$$\begin{aligned}A + \bar{A}B &= (A + AB) + \bar{A}B \\&= (AA + AB) + \bar{A}B \\&= AA + AB + A\bar{A} + \bar{A}B \\&= (A + \bar{A})(A + B) \\&= 1 \cdot (A + B) \\&= A + B\end{aligned}$$

- Rule 12:  $(A + B)(A + C) = A + BC$

$$\begin{aligned}(A + B)(A + C) &= AA + AC + AB + BC \\&= A + AC + AB + BC \\&= A(1 + C) + AB + BC \\&= A \cdot 1 + AB + BC \\&= A(1 + B) + BC \\&= A \cdot 1 + BC \\&= A + BC\end{aligned}$$
 
# Rules of Boolean Algebra

- DeMorgan's first theorem  $\overline{XY} = \overline{X} + \overline{Y}$




Inputs		Output	
X	Y	$\overline{XY}$	$\overline{X} + \overline{Y}$
0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0

Think about it:

- 3 variable DeMorgan's Theorems?

 - DeMorgan's second theorem  $\overline{\overline{X} + \overline{Y}} = \overline{X} \overline{Y}$



Inputs		Output	
X	Y	$\overline{\overline{X} + \overline{Y}}$	$\overline{X} \overline{Y}$
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0

- DeMorgan's theorems provide mathematical equivalency of the NAND and negative-OR gates and the equivalency of the NOR and negative-AND gates



# Rules of Boolean Algebra

- 代入定理

在任何一个包含变量A的逻辑等式中，若以另外一个逻辑式代入式中所有A的位置，则等式仍然成立

e.g., 3 variable DeMorgan's Theorems?

- 反演定理

对于任意一个逻辑式Y，若将其中所有的·换成+，+换成·，0换成1，1换成0，原变量换成反变量，反变量换成原变量，则得到的结果就是Y'

$$Y=A(B+C)+CD \quad \longrightarrow \quad Y'=(A'+B'C')(C'+D')$$

- 对偶定理

若两逻辑式相等，则它们的对偶式也相等

对偶式：对于任何一个逻辑式Y，若将其中的·换成+，+换成·，0换成1，1换成0，则得到Y的对偶式Y<sup>D</sup>。

$$Y=A+BC \quad \longrightarrow \quad Y^D=A(B+C)$$

$$Y=(A+B)(A+C) \quad \longrightarrow \quad Y^D=AB+AC$$

Exercise:

$$(AB + AC)' + A'B'C$$



# Midterm 2025



- (a) (\_\_\_\_) How many input variable combinations does a four-input **NOR** gate have that result in an output of 1?
- A. 15.
  - B. 8.
  - C. 7.
  - D. 1.
- (b) **(Multiple Choice)** (\_\_\_\_\_) Which of the following statement(s) are(is) true about boolean algebra? (where  $\oplus$  denotes **XOR**)
- A.  $X(Y \oplus Z) = (XY) \oplus (XZ)$ .
  - B.  $(X \oplus \bar{Y}) \oplus Z = X \oplus (\bar{Y} \oplus Z)$ .
  - C.  $X + YZ = (X + Y)(X + Z)(\bar{X} + Y + Z)$ .
  - D.  $(X + Y)(\bar{X} + Z)(Y + Z) = (X + Y)(\bar{X} + Z)$ .



# Midterm 2025



- (c) (\_\_\_\_) Build a logic circuit with only 2-input **AND** and 2-input **OR** gates to implement the function shown in the truth table below. What are the minimal numbers of needed **AND** gates and **OR** gates?

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

- A. 3 **AND** gates and 3 **OR** gates.
- B. 3 **AND** gates and 2 **OR** gates.
- C. 2 **AND** gates and 3 **OR** gates.
- D. 2 **AND** gates and 2 **OR** gates.
- E. 2 **AND** gates and 1 **OR** gate.
- F. 1 **AND** gate and 2 **OR** gates.



# Midterm 2024



(a) **(Multiple Choice)** Which of the following statement(s) are(is) true about boolean algebra? (            )


A.  $X + YZ = (X + Y)(X + Z)$

B.  $(X + \bar{Y})X = X + X\bar{Y}$

C.  $XY + X = X$

D.  $\overline{XY} = \bar{X} + \bar{Y}$

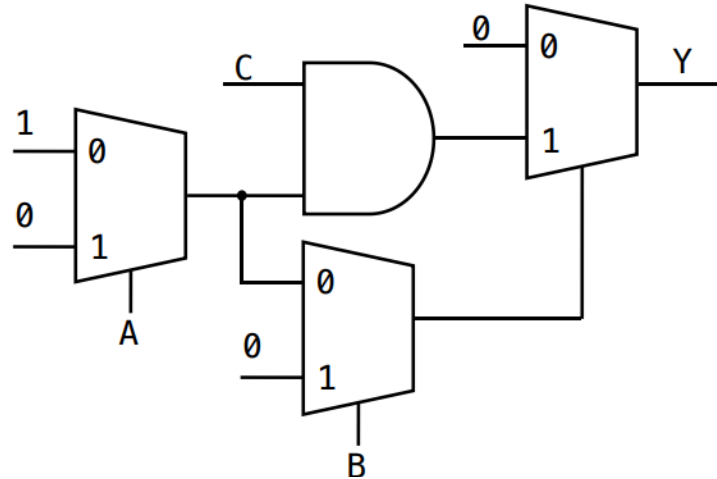(b) The following circuit is composed of several basic logic gates and 2-to-1 multiplexers. Please write down the truth table of the circuit below.



(c) Write down the logic expression that implements the truth table using sum of minterm.

Build a logic circuit that uses only 2-input **AND**, 2-input **OR** and **NOT** gates implementing the same logic above. Use as less logic gates as possible.




# Midterm 2024



Truth Table

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

$$Y = \bar{A}\bar{B}C.$$


 


- ❑ Learn difference of Moore machine and Mealy machine
- ❑ Be able to write the truth table
- ❑ Be able to draw FSM transition diagram
- ❑ Be able to deduce the evolution of FSM

# Moore machine

## Moore machine vs. Mealy machine

- Moore machine

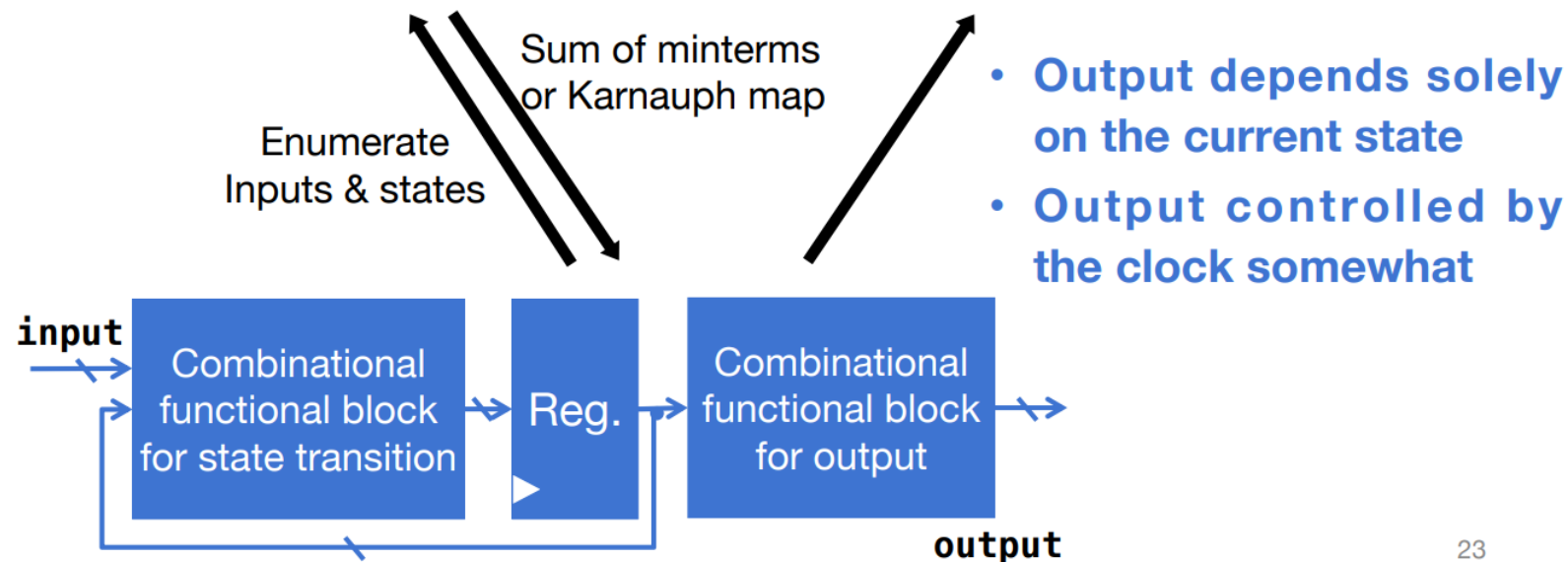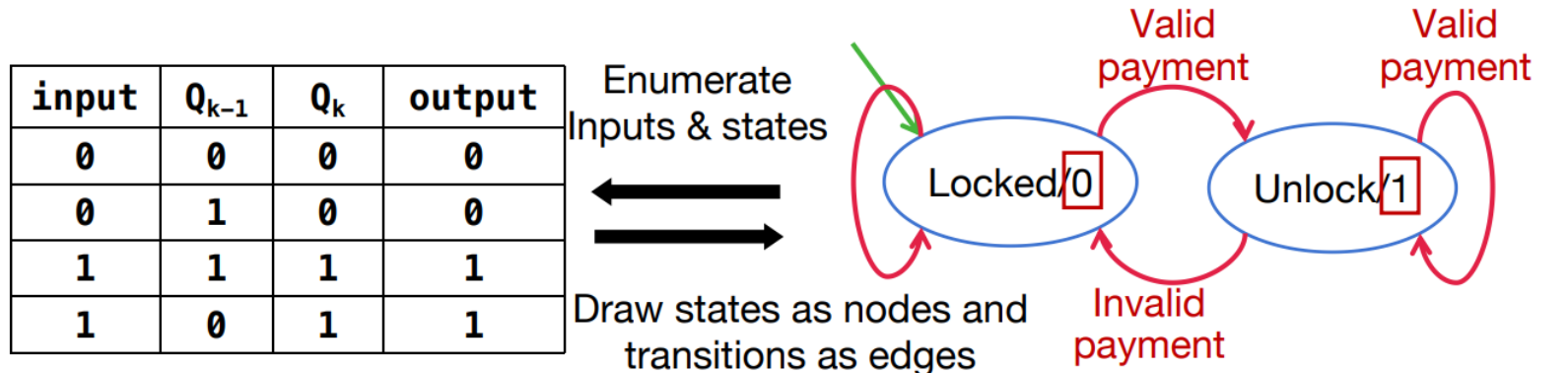


# Mealy machine

## Moore machine vs. Mealy machine

- Mealy machine


input	$Q_{k-1}$	$Q_k$	output
0	0	0	0
0	1	0	0
1	1	1	1
1	0	1	1

Enumerate  
Inputs & states

 

Sum of minterms  
or Karnaugh map

Enumerate  
Inputs & states

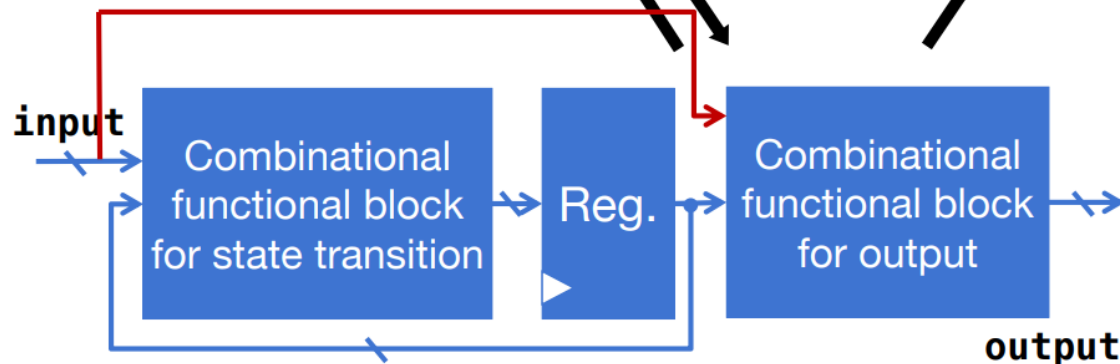

- Output depends on both the current state **and** input
- Output uncontrolled by the clock
- Mealy and Moore machines are interchangeable
- Mealy and Moore outputs can co-exist in one synchronous circuit

# Timing




- Learn definition of the  $t_{\text{clk-to-Q}}$ ,  $t_{\text{comp}}$ , setup time and Hold time
- Know the constraints for the max frequency(min period)
- Be able to Find critical path
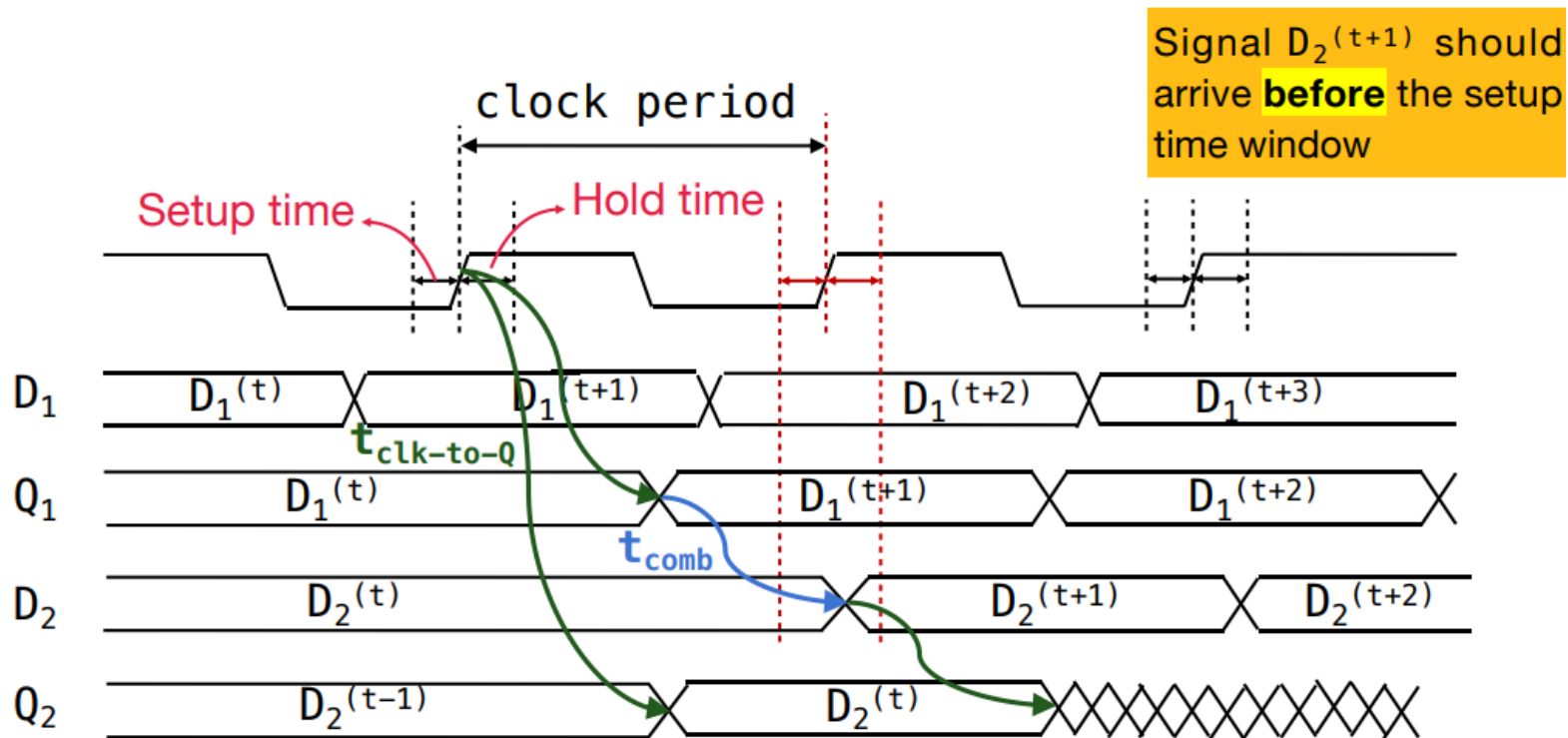
## Estimating the max frequency

Max frequency =  $1/\text{min clock period}$

$$t_{\text{clk-to-Q}} + t_{\text{comb}} \leq \text{min clock period} - \text{setup time}$$






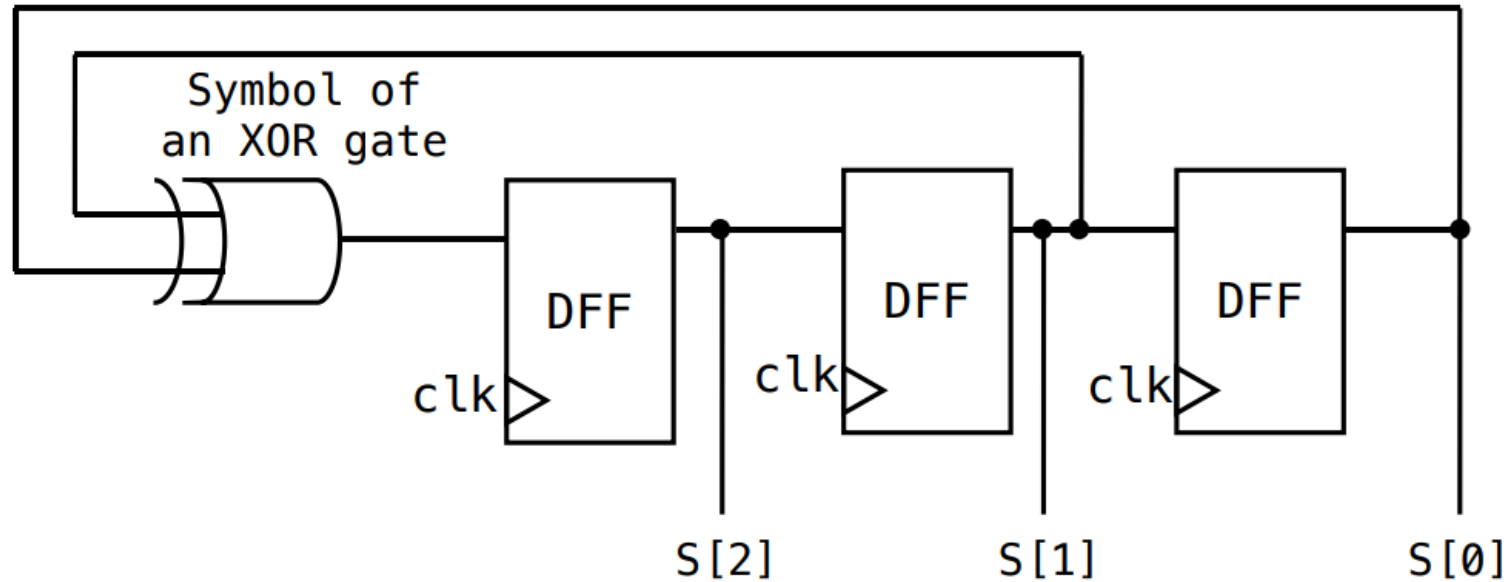
# Midterm 2024



Below shows a synchronous circuit called linear feedback shift register (LFSR), consisting of one or more **XOR** gates and several DFFs. It has been widely used for generating pseudorandom numbers. It can be modeled by a finite state machine (FSM) like the other synchronous circuits, however, without any input signals. Given the current state  $S_{k-1}$ , fill in the truth table of its next state  $S_k$ .  $S$  is a 3-bit signal.



# Midterm 2024

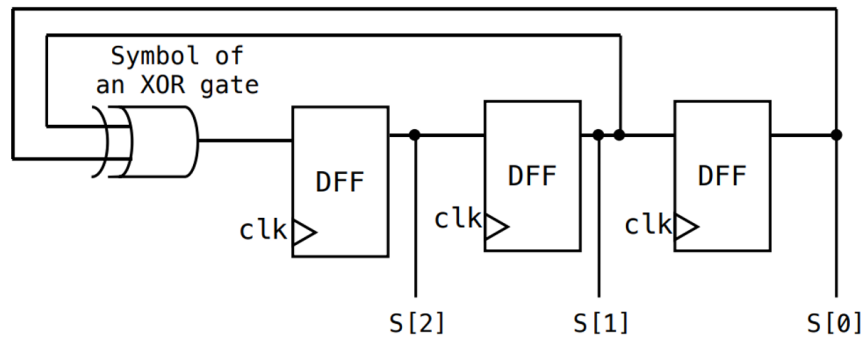

Truth Table

$S[2]_{k-1}$	$S[1]_{k-1}$	$S[0]_{k-1}$	$S[2]_k$	$S[1]_k$	$S[0]_k$
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	0	1
0	1	1	0	0	1
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	1	1



# Midterm 2024




For the above FSM, we use the unsigned number  $(S[2]S[1]S[0])_2$  to represent its state and output. Please complete the state transition diagram below. Tips: This FSM has no input, and we do not put the transition condition on the transition edges or lines. Also, we use “0/0” to denote that the FSM is currently at state 0 and its output is 0, respectively.


 
# Midterm 2024



For the above FSM, we use the unsigned number  $(S[2]S[1]S[0])_2$  to represent its state and output. Please complete the state transition diagram below. Tips: This FSM has no input, and we do not put the transition condition on the transition edges or lines. Also, we use “0/0” to denote that the FSM is currently at state 0 and its output is 0, respectively.





# Midterm 2024



The setup time of a DFF is 1 ns, the delay of an **XOR** gate is 2 ns, and the **clk-to-q** delay of the DFF is 1 ns. Compute the maximum frequency of this circuit. (We ignore the delay of the lines and ignore all the other non-ideal effects such as clock skews, etc.)



# Midterm 2024



The setup time of a DFF is 1 ns, the delay of an **XOR** gate is 2 ns, and the **clk-to-q** delay of the DFF is 1 ns. Compute the maximum frequency of this circuit. (We ignore the delay of the lines and ignore all the other non-ideal effects such as clock skews, etc.)

**Solution:** Critical path = XOR delay + DFF setup time + DFF clk-to-q delay = 4 ns  
(2 marks)

Max. frequency =  $1/\text{Critical path} = 250 \text{ MHz}$  or  $0.25 \text{ GHz}$  (1 mark, if you only have this result but not calculating critical path, you also get full marks.)

# Thanks!



---

## Reference

CS110\_2023\_MidtermExam\_I

CS110\_2024\_MidtermExam\_I

CS110\_2025\_MidtermExam\_I

EE115

Discussion6 2025 ( by Yutong Wang)





# Midterm 2023



Truth table:

A	B	C	D	Output
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1


Karnaugh map:

		AB			
		00	01	11	10
CD	00	0	0	0	1
	01	0	0	0	1
	11	1	1	1	1
	10	1	1	1	1

$$(\overline{A}\overline{B} + C)D + A(\overline{B + D}) + \overline{\overline{C} + D} = \overline{A}\overline{B}D + CD + \overline{A}\overline{B}\overline{D} + C\overline{D} = \overline{A}\overline{B} + C$$



# Midterm 2023

 


Below shows a state transition diagram of a finite state machine (FSM) with 4 states. What is the type of the FSM?

- A. A Moore machine.
- B. A Mealy machine.

Assume the input bit sequence to the FSM is 10011010, the output is .

Which state does the FSM arrive at last?\_

# Midterm 2023

 

Below shows a state transition diagram of a finite state machine (FSM) with 4 states.

What is the type of the FSM?

A. A Moore machine.

▲ B. A Mealy machine.

Assume the input bit sequence to the FSM is 10011010, the output is\_.

**Solution:** 00101000.

Which state does the FSM arrive at last?\_


**Solution:** A.


 
# Midterm 2023




- Build a **Moore** FSM model to detect “010” pattern in a bit sequence (use overlapping, i.e., the tail 0 of “010” can be considered as the head 0 for the next detection). The states are given below. Please complete the state transition diagram by adding the transitions, transition conditions and output for each state. [4 points]


 
# Midterm 2023



- Build a **Moore** FSM model to detect “010” pattern in a bit sequence (use overlapping, i.e., the tail 0 of “010” can be considered as the head 0 for the next detection). The states are given below. Please complete the state transition diagram by adding the transitions, transition conditions and output for each state. [4 points]





# Midterm 2023



(e) Assign “00” (0) to represent state “Start over”, “01” (1) to represent “{0} detected”, “10” (2) to represent “{01} detected” and “11” (3) to represent “{010} detected”. Write down the truth table for the next-state and output logic. We use “CS” to represent current state and “NS” for next state.

CS[1]	CS[0]	input	NS[1]	NS[0]	output
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			



# Midterm 2023



- (e) Assign “00” (0) to represent state “Start over”, “01” (1) to represent “{0} detected”, “10” (2) to represent “{01} detected” and “11” (3) to represent “{010} detected”. Write down the truth table for the next-state and output logic. We use “CS” to represent current state and “NS” for next state.

CS[1]	CS[0]	input	NS[1]	NS[0]	output
0	0	0	0	1	0
0	0	1	0	0	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	1	0
1	0	1	0	0	0
1	1	0	0	1	1
1	1	1	1	0	1


Complete the circuit below for the “010” sequence detection task using the truth table you just wrote.


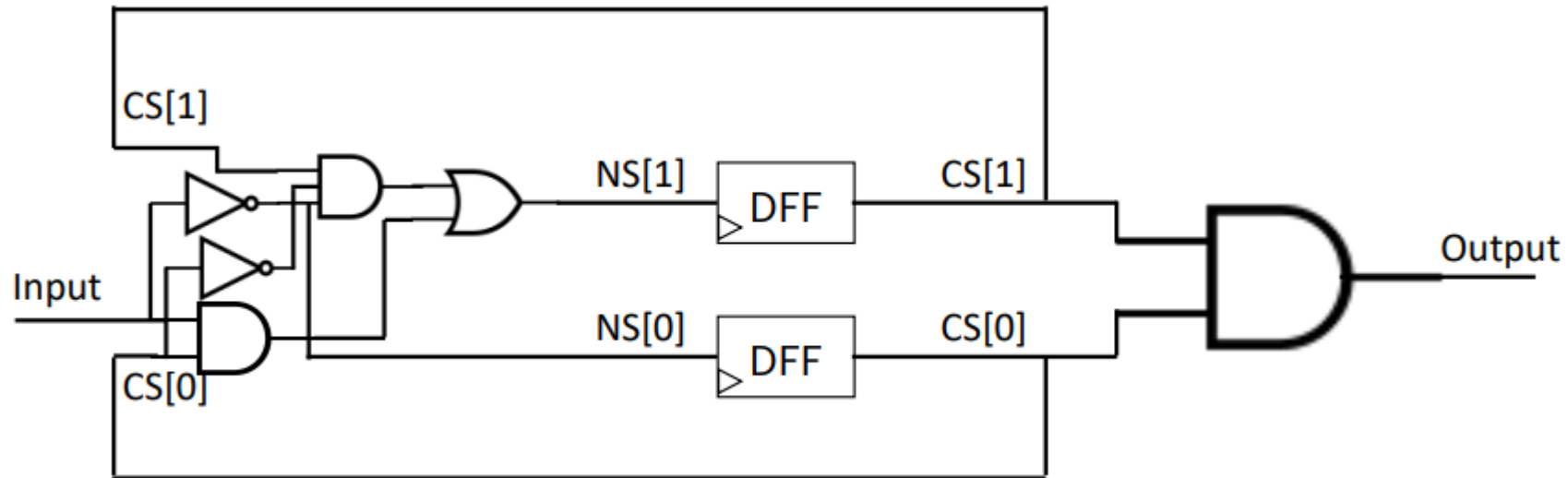
# Midterm 2023




Complete the circuit below for the “010” sequence detection task using the truth table you just wrote.



# Midterm 2023



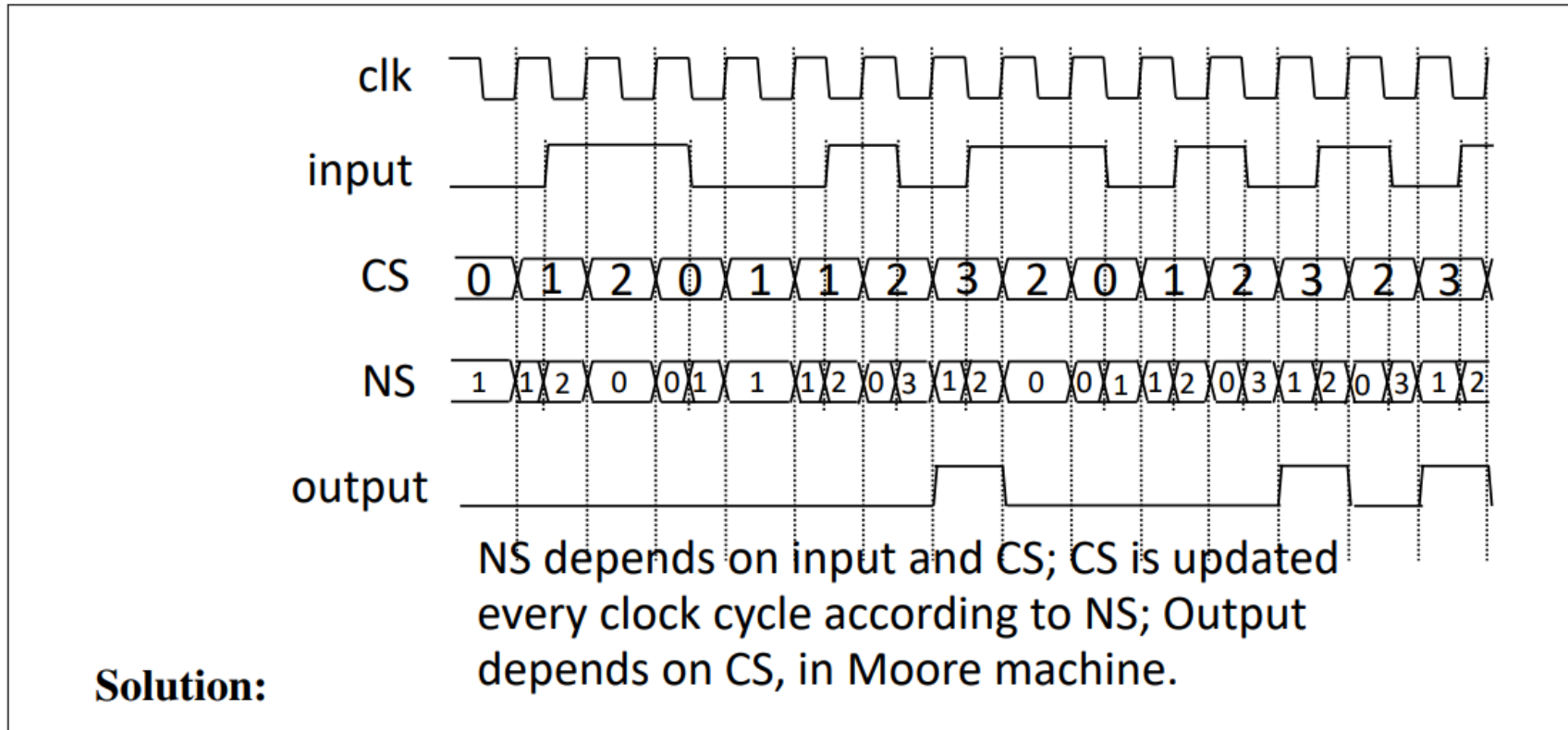(g) Draw the timing diagram given the clock signal and input below. We ignore the non-ideal effects, and integers (use signal grouping) are used to represent the states.





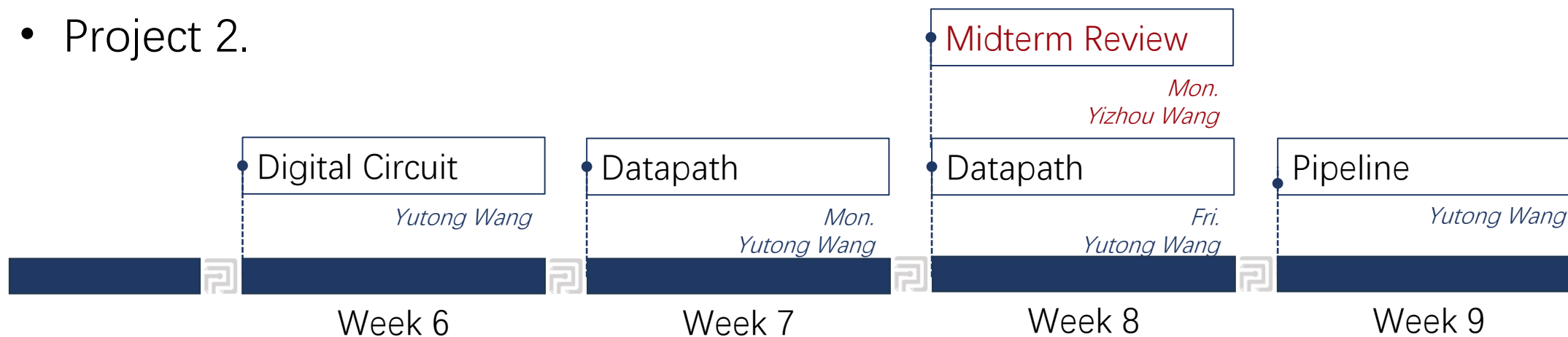
# Schedule

This section includes:

- Lab 5, Lab 6, Lab8;
- Homework 4;
- Project 2.



Midterm Exam I!  
Project 2.1 will release after exam.

We strongly recommend that you start reviewing as soon as possible!