



信息科学与技术学院

School of Information Science and Technology

CS 110

Computer Architecture

Digital Circuits and Systems

Instructors:

Siting Liu & Yuan Xiao

Course website: <https://faculty.sist.shanghaitech.edu.cn/liust/courses/CS110.html>

School of Information Science and Technology (SIST)

ShanghaiTech University

2026/3/31

Administratives

- HW3 released, ddl Apr. 9th!
 - Only those submissions before ddl will receive marks, otherwise you got 0. So **START EARLY!**
 - Make sure you submit the **correct activated version!**
- Lab 5 will be available today (logisim), please prepare in advance, check next week! Lab 4 to check this week.
- Proj 1.1 released, ddl Apr. 7th.
- Discussion this week on RISC-V calling convention by TA Letong Han at SPST 4-122 18:00-19:40.

Outline

- **Digital system**
- **Combinational logics**
 - From transistors to basic logic gates
 - From logic gates to combinational circuits
 - Boolean algebra
 - Boolean expression
 - Truth table
- State elements
- Useful building blocks

Where are we?

High Level Language Program (e.g., C)

Compiler

Assembly Language Program (e.g., RISC-V)

Assembler

Machine Language Program (RISC-V)

```
temp = v[k];  
v[k] = v[k+1];  
v[k+1] = temp;
```

```
lw    t0, 0(s2)  
lw    t1, 4(s2)  
sw    t1, 0(s2)  
sw    t0, 4(s2)
```


```
0000 1001 1100 0110 1010 1111 0101 1000  
1010 1111 0101 1000 0000 1001 1100 0110  
1100 0110 1010 1111 0101 1000 0000 1001  
0101 1000 0000 1001 1100 0110 1010 1111
```

Machine Interpretation

Hardware Architecture Description (e.g., block diagrams)

Architecture Implementation

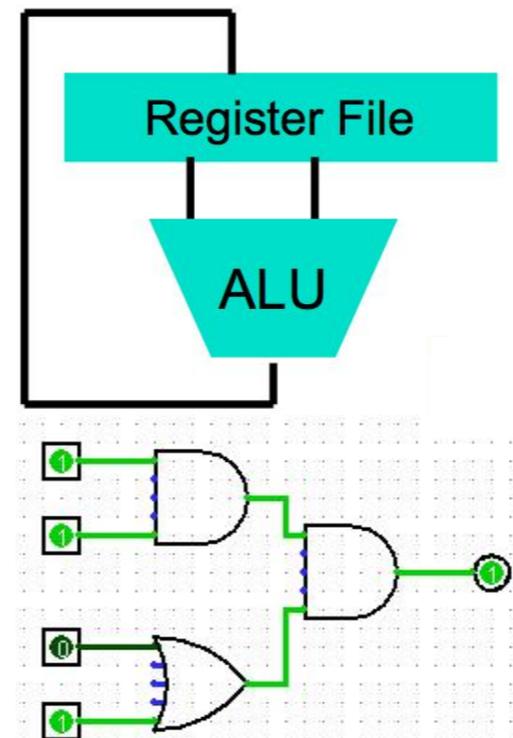Logic Circuit Description (Circuit Schematic Diagrams)




We are here!

Bottom-up

Hardware (HW) Design


- Next several weeks: how a modern processor is built, starting with basic elements (transistors) as building blocks
- Why study hardware design?
 - Understand capabilities and limitations of HW in general and processors in particular
 - What processors can do fast and what they can't do fast (avoid slow things if you want your code to run fast!)
 - Background for more in-depth HW courses (Digital circuit/VLSI/AI computing system, etc.)
 - There is only so much you can do with standard processors: you may need to design own custom HW for extra performance
 - Even some commercial processors today have customizable hardware!
 - E.g. Google Tensor Processing Unit (TPU), NVIDIA Groq language processing unit (LPU)

Components of Computers

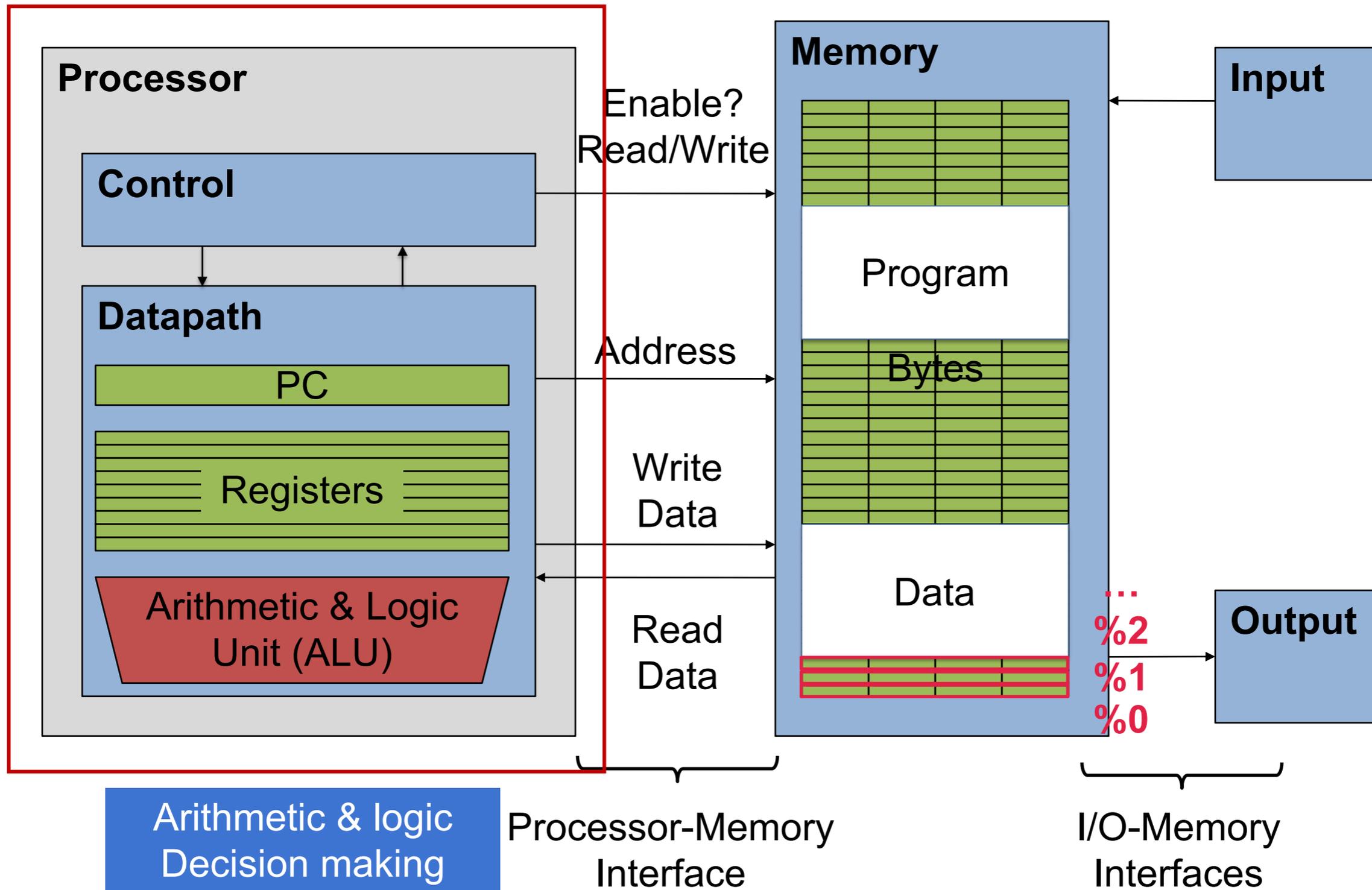


Switches: Basic Element of Physical Implementations

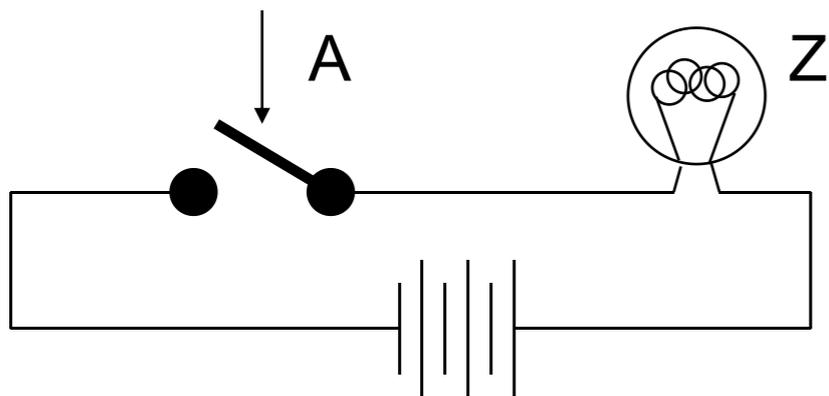- Implementing a simple circuit (arrow shows action if wire changes to “1” or is *asserted*):



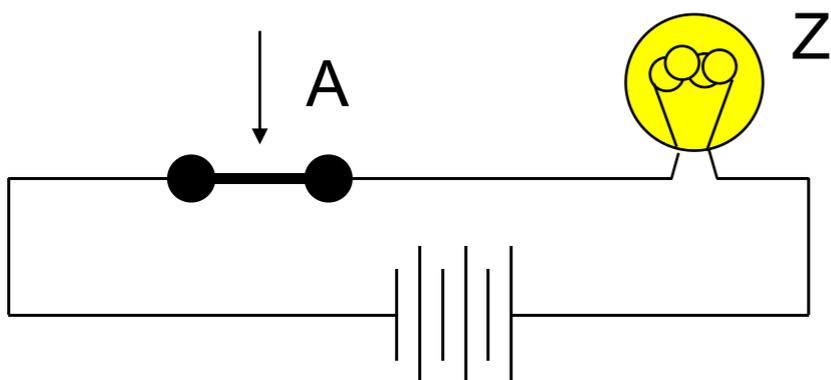Off-switch (if A is “0” or unasserted) turns-off light bulb (Z)




On-switch (if A is “1” or asserted) turns-on light bulb (Z)


$$Z = A$$

Switches

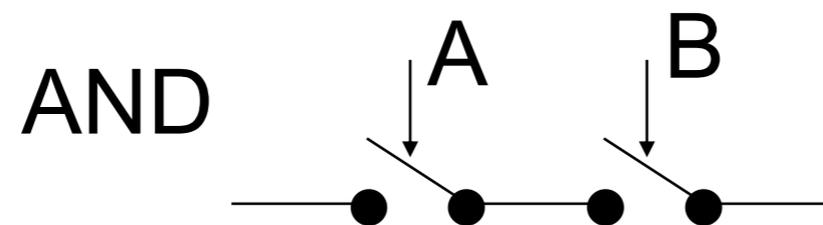- Compose switches into more complex ones (Boolean functions):




$$Z = A \text{ and B}$$

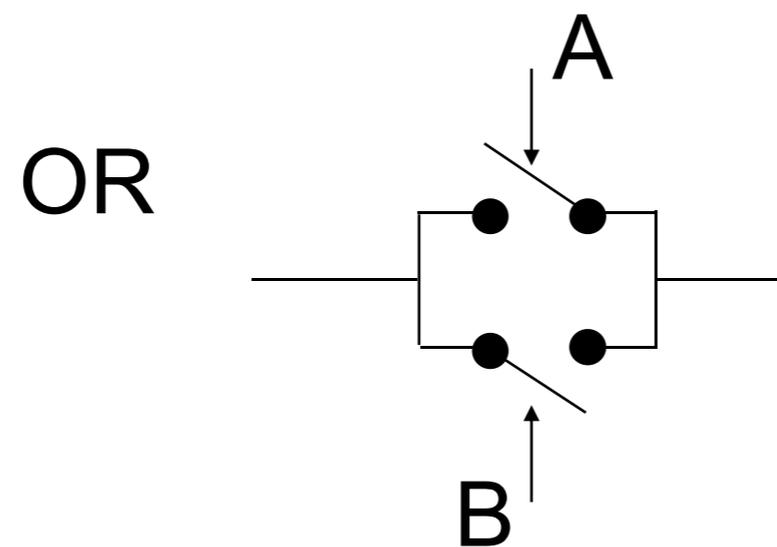

$$Z = A \text{ or B}$$


Revisit: Binary System

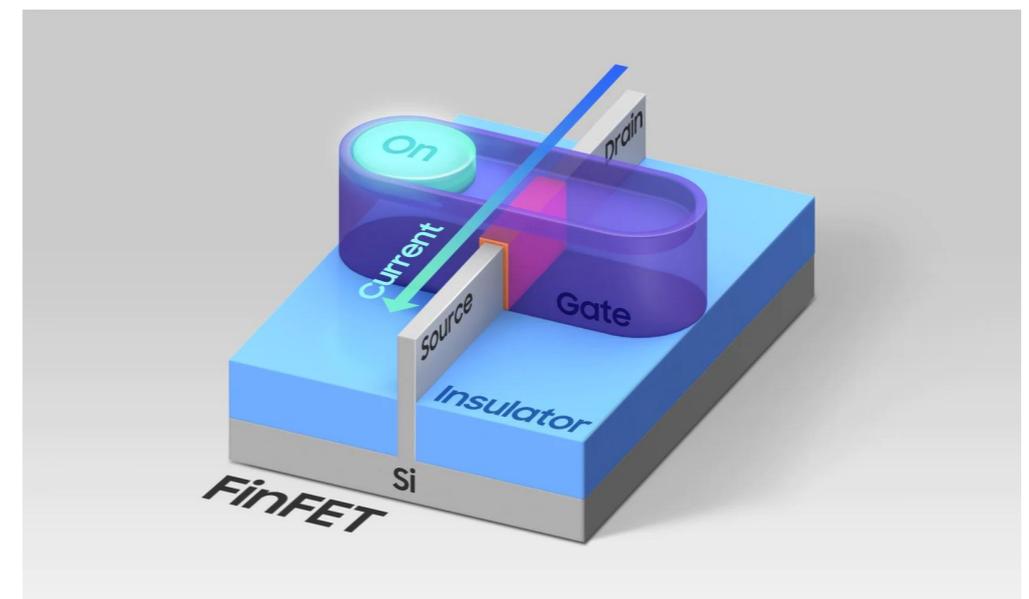- 0 and 1 (binary digit or bit, unit of information entropy)
- Decided by the characteristic of semiconductor devices (bi-stable states)
 - **They can also be considered as voltage-controlled switches**
- Resilient to noise (threshold)
- Supported by Boolean algebra theory (George Boole, 1854)
- Basic operations: \wedge , \vee , \sim (Universal set)



Binary Representation of Signals



- High voltage (V_{dd}) represents 1, or true
 - In modern microprocessors, core $V_{dd} \sim 1.0$ Volt
- Low voltage (0 Volt or Ground) represents 0, or false
- **Digital**: discretize signal/voltage to a 0 or a 1
 - This removes noise as signals propagate – a big advantage of digital systems over **analog** systems
 - Circuits to discriminate between two possible inputs are simple to implement and have scaled well with Moore's Law.
- If one switch can control another switch with digital signal, we can build a computer!
- Our switches: CMOS transistors

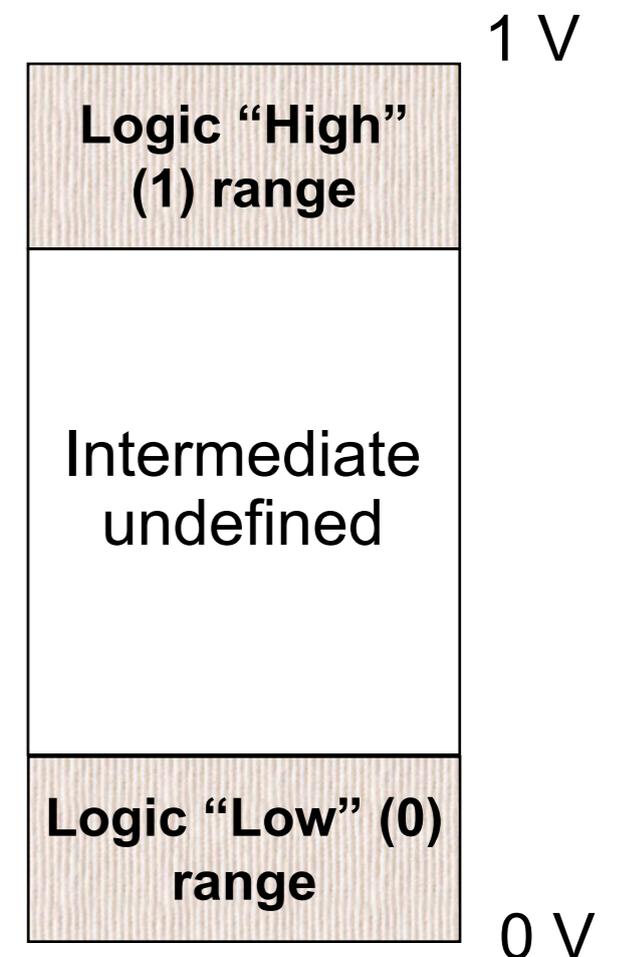

Abstraction

NMOS & PMOS Transistors

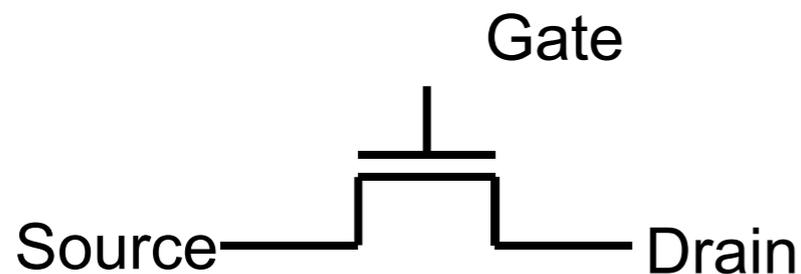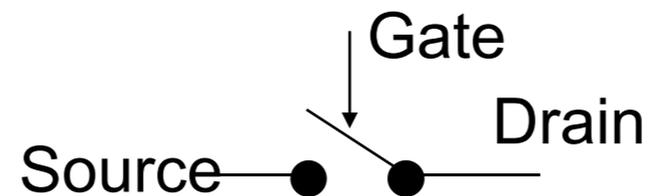- Three terminals: source, gate, and drain
 - Basic model




n-channel transistor

off when voltage at Gate is low

on when:

voltage (Gate) > voltage (Threshold)

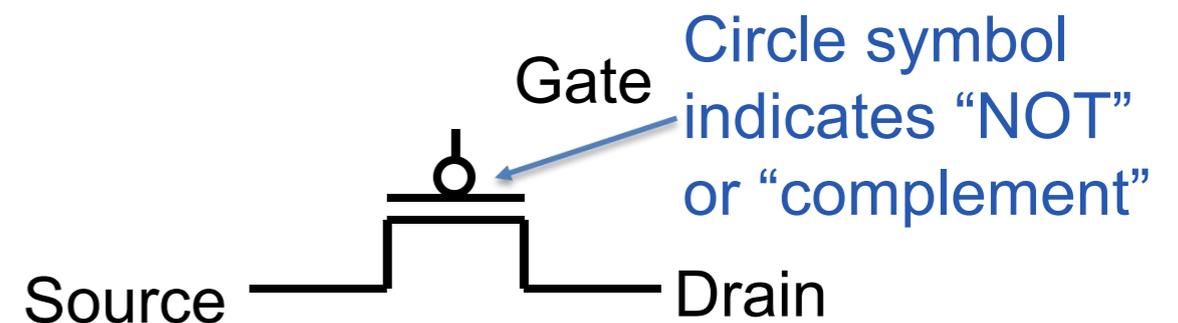(High resistance when gate voltage Low,
Low resistance when gate voltage High)



p-channel transistor

on when voltage at Gate is low

off when:


voltage (Gate) > voltage (Threshold)

(Low resistance when gate voltage Low,
High resistance when gate voltage High)


NMOS & PMOS Transistors: Clarifications

- Transistors can be modeled by resistors and capacitors, i.e., they can have non-ideal effects such as **leakage** and **delay**
- Recent trend of transistors
- Real stuff: AMD Zen 2

Planar → FinFET → GAAFET

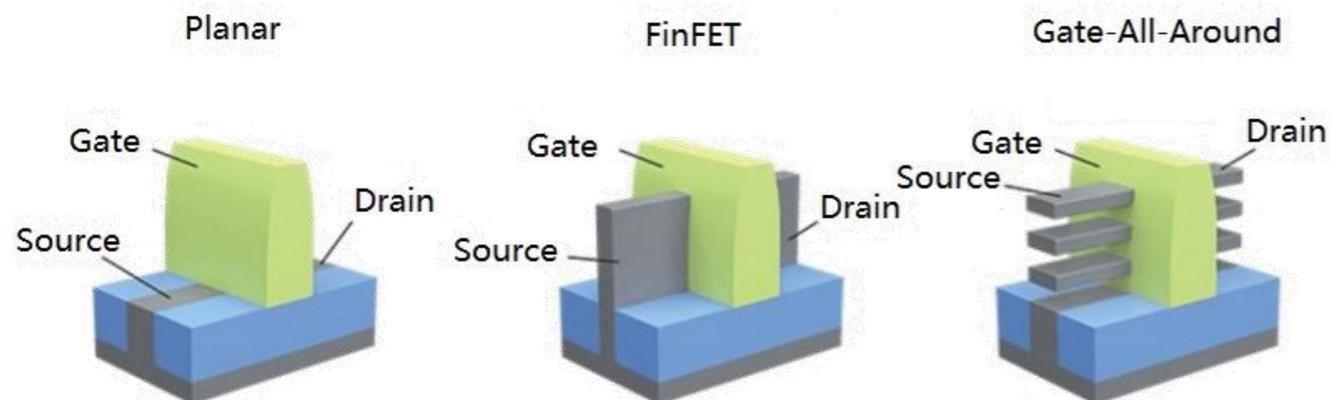

From Utmel.com

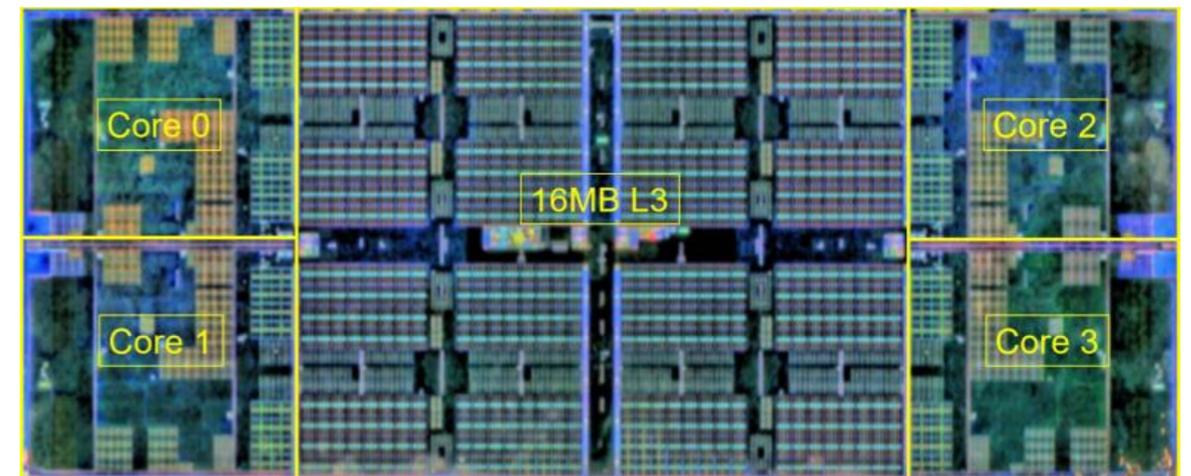


475M-transistor core slice is 7.83mm^2 with a 0.5MB L2 cache and 4MB of shared L3 cache

Synchronous Digital System (SDS)



- A system that processes digital signals (0's and 1's)
- Synchronous digital systems consist of two basic types of circuits.
 - Combinational logic circuits (**this lecture**)
 - The outputs solely depend on the input
 - No way to store information
 - State Elements (next lecture)
 - Circuits that store information
 - E.g., registers and memory
- CPU cores are SDS's
 - Our Goal: Implement a RISC-V processor as a synchronous digital system.
 - This SDS should have the capabilities to execute RISC-V instructions.

From Transistors to Logic Gates

- **Complementary MOS (CMOS)**

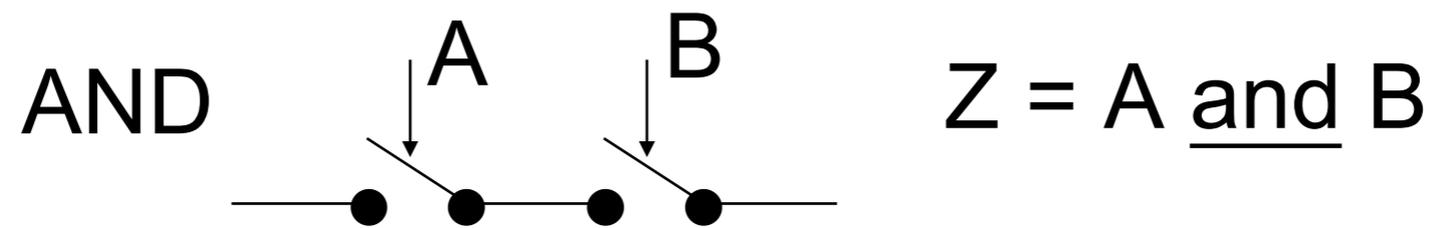


Similarly

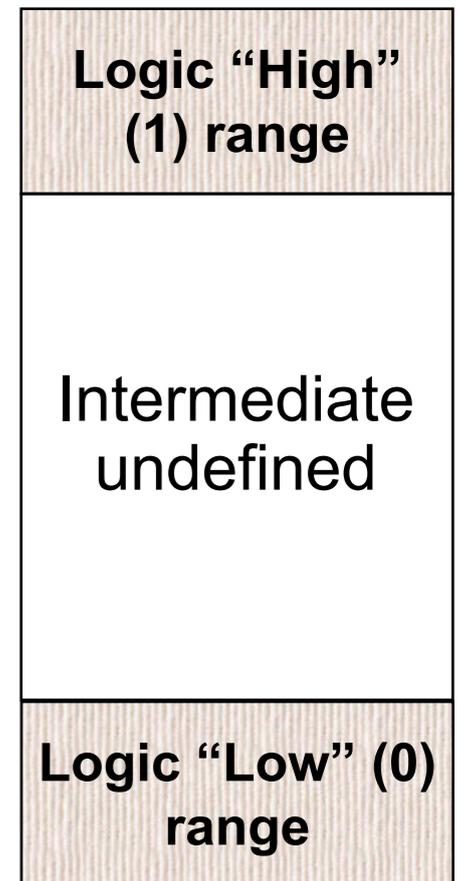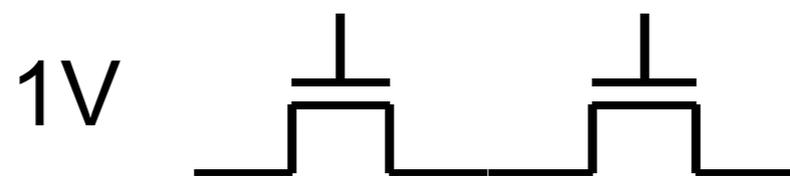

- N-type transistors (NMOS) pass weak 1 ($V_{dd} - V_{th}$) and strong 0
- P-type transistors (PMOS) pass weak 0 (V_{th}) and strong 1
- **Abstraction not accurate enough**
- **FIX:** Pairs of N/P-type transistors to pass strong 0 and strong 1 (CMOS)

The Simplest CMOS Circuits

- Inverter/Not gate

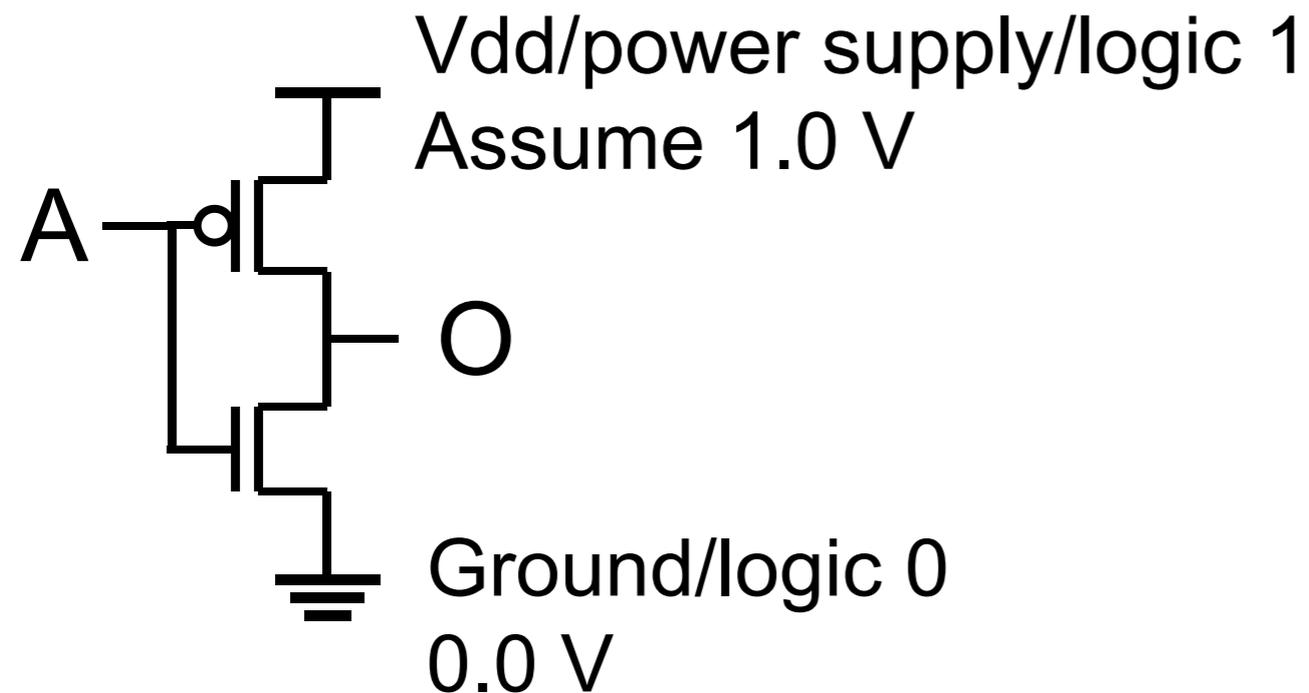

$O = \text{not } A$


Truth table

A	O
0	1
1	0

AND Gate

Truth table

A	B	O
0	0	0
0	1	0
1	0	0
1	1	1

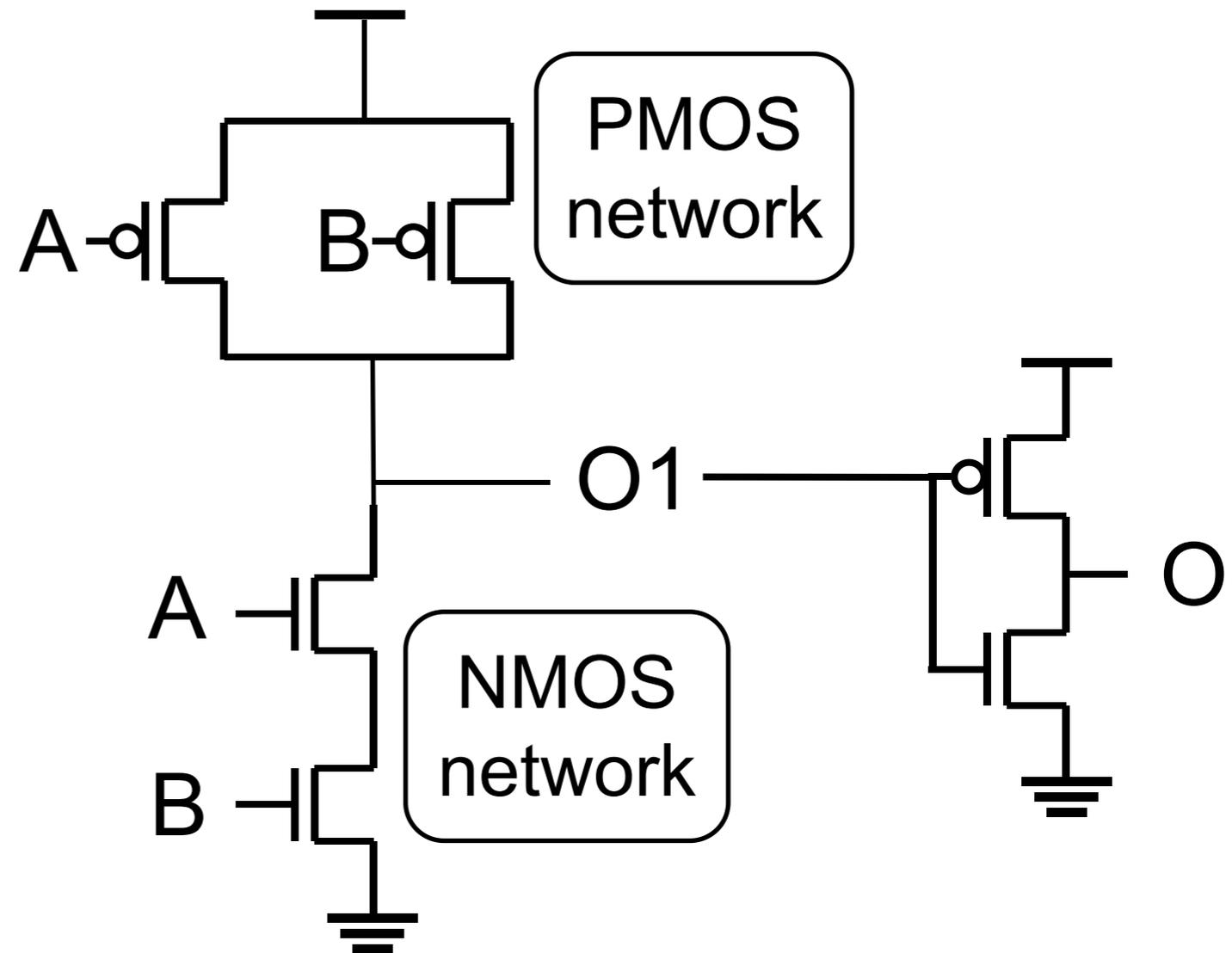


What about 3-input AND?

What about 2-input NAND?

OR Gate


Truth table

A	B	O
0	0	0
0	1	1
1	0	1
1	1	1

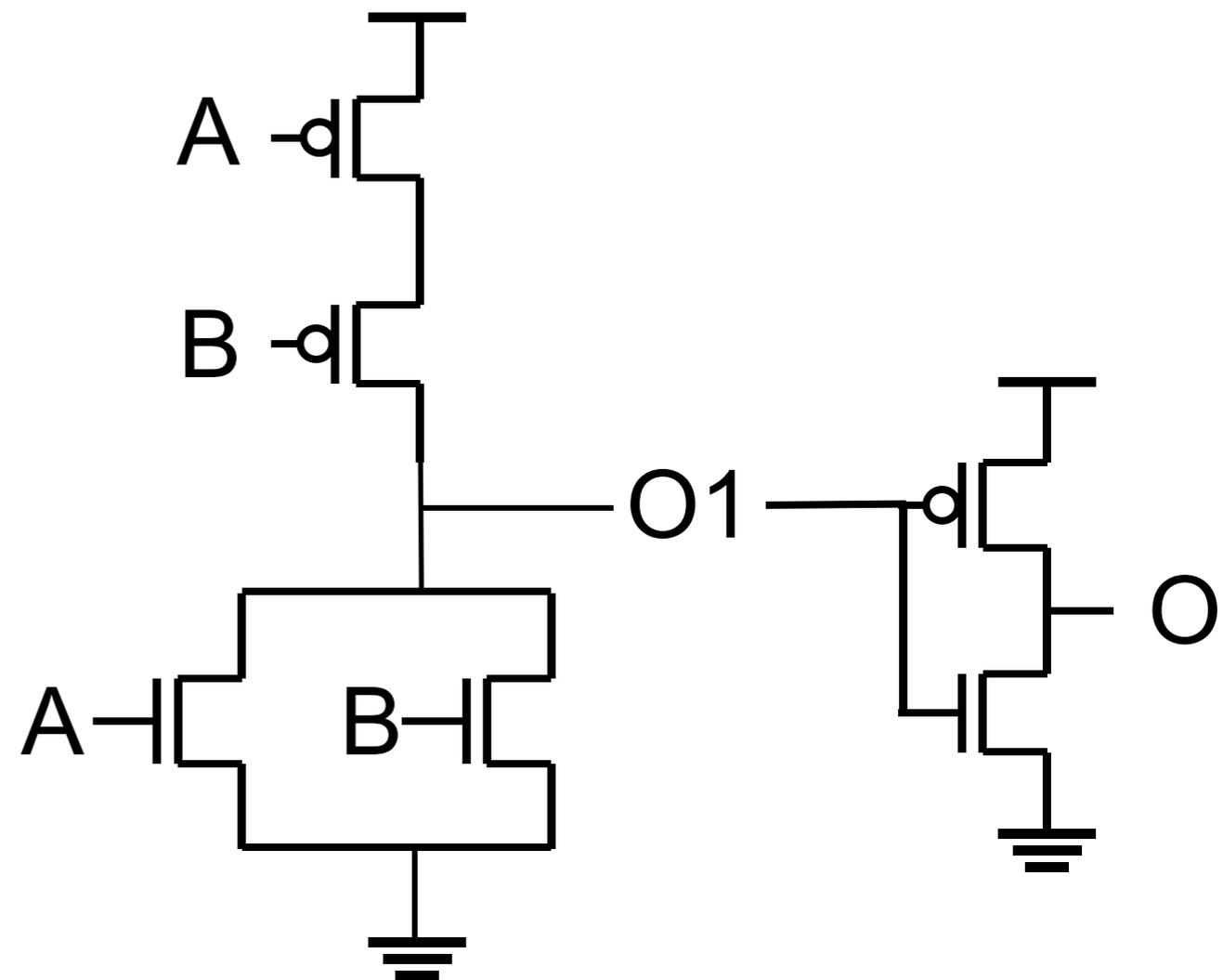

What about 3-input OR?


General CMOS Logic Gates

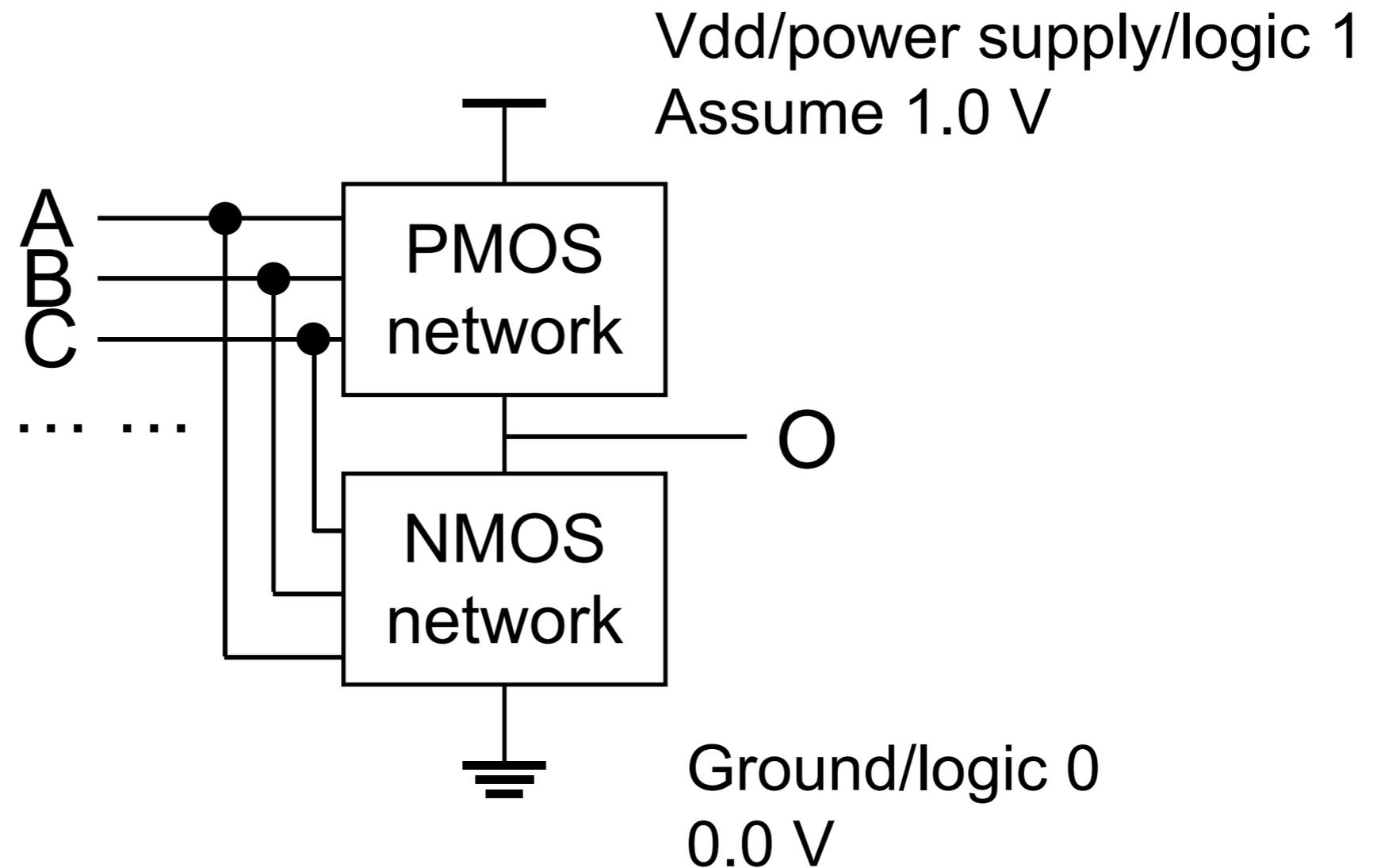

Basic Symbols

- Standard symbols for logic gates

– Buffer, NOT

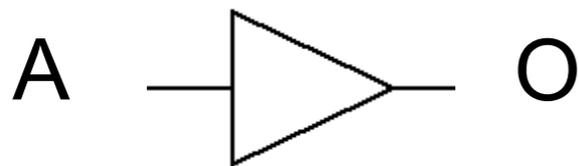

- Universal sets

– NOT, AND, OR

Can be combined to implement any logics

– AND, NAND



– NAND

– OR, NOR



– NOR

Through Boolean algebra!

From Logic Gates to Building Blocks

- Method 1: through boolean expressions (sum-of-minterm)
- Method 2: Karnaugh Map
 - Go to SI100I

Boolean Algebra

- Use plus “+” for OR
 - “logical sum” $1+0=0+1=1$ (True); $1+1=2$ (True); $0+0=0$ (False)
- Use product for AND ($a \cdot b$ or implied via ab)
 - “logical product” $0 \cdot 0 = 0 \cdot 1 = 1 \cdot 0 = 0$ (False); $1 \cdot 1 = 1$ (True)
- “Bar” to mean complement (NOT)
- Thus
$$ab + a + \bar{c}$$
$$= a \cdot b + a + \bar{c}$$
$$= (a \text{ AND } b) \text{ OR } a \text{ OR } (\text{NOT } c)$$



Build Combinational Circuits with Basic Logic Gates

- Combinational circuits: the ones that the output of the digital circuits depends solely on its inputs; usually built with logic gates without feedback
 - **Step 1:** Write down truth table of the desired logic

For example build an XOR
with AND/OR/NOT

A	B	O
0	0	0
0	1	1
1	0	1
1	1	0

Build Combinational Circuits with Basic Logic Gates

- Combinational circuits: the ones that the output of the digital circuits depends solely on its inputs; usually built with logic gates without feedback
 - Step 2:** Pick the lines with 1 as the output; write them down in *Sum of Minterms (Product)* form;

For example build an XOR with AND/OR/NOT

A	B	O
0	0	0
0	1	1
1	0	1
1	1	0

Minterms

$\overline{A} \overline{B}$	m_0
$\overline{A} B$	m_1
$A \overline{B}$	m_2
$A B$	m_3

Build Combinational Circuits with Basic Logic Gates

- Combinational circuits: the ones that the output of the digital circuits depends solely on its inputs; usually built with logic gates without feedback
 - Step 3:** Simplify using Laws of Boolean algebra;

For example build an XOR with AND/OR/NOT

A	B	O
0	0	0
0	1	1
1	0	1
1	1	0

$$O = m_1 + m_2$$

Minterms

$\overline{A}\overline{B}$	m_0
$\overline{A}B$	m_1
$A\overline{B}$	m_2
AB	m_3

Laws of Boolean Algebra

AND form

$$X\bar{X} = 0$$

$$X0 = 0$$

$$X1 = X$$

$$XX = X$$

$$XY = YX$$

$$(XY)Z = X(YZ)$$

$$X(Y+Z) = XY+XZ$$

$$\overline{XY+X} = \bar{X}$$

$$\overline{XY} = \bar{X}+\bar{Y}$$

OR form

$$X+\bar{X} = 1$$

$$X+1 = 1$$

$$X+0 = X$$

$$X+X = X$$

$$X+Y = Y+X$$

$$(X+Y)+Z = X+(Y+Z)$$

$$X+YZ = (X+Y)(X+Z)$$

$$\overline{(X+Y)X} = \bar{X}$$

$$\overline{X+Y} = \bar{X}\bar{Y}$$

Complementarity
Laws of 0's and 1's
Identities
Idempotent Laws
Commutativity
Associativity
Distribution
Absorption
DeMorgan's Law

Building Blocks


- Build a half adder:

	Sum	Carry
• $0 + 0 = 0$	0	0
• $0 + 1 = 1$	1	0
• $1 + 0 = 1$	1	0
• $1 + 1 = 0$	0	1

- Build a 2-bit adder:

	Sum	Carry		Sum	Carry
• $00 + 00 = 00$	00	0	• $10 + 00 = 10$	10	0
• $00 + 01 = 01$	01	0	• $10 + 01 = 11$	11	0
• $00 + 10 = 10$	10	0	• $10 + 10 = 00$	00	1
• $00 + 11 = 11$	11	0	• $10 + 11 = 01$	01	1
• $01 + 00 = 01$	01	0	• $11 + 00 = 11$	11	0
• $01 + 01 = 10$	10	0	• $11 + 01 = 00$	00	1
• $01 + 10 = 11$	11	0	• $11 + 10 = 01$	01	1
• $01 + 11 = 00$	00	1	• $11 + 11 = 10$	10	1
	AB	CD			


Another Method—Karnaugh Map (optional)

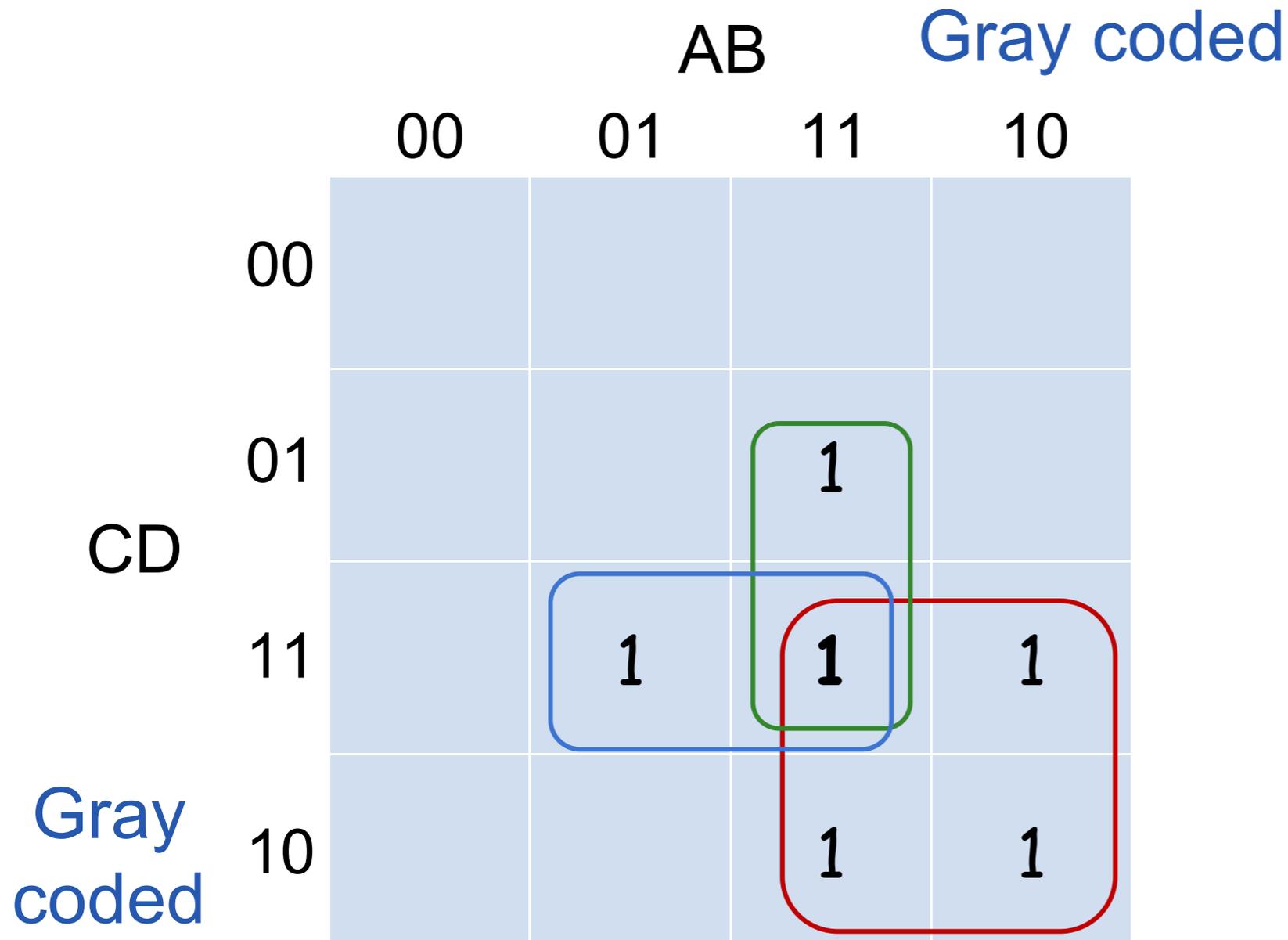

Each cell corresponds to a minterm

Online Karnaugh map solver: <http://www.32x8.com/index.html>

Representations of Combinational Logic

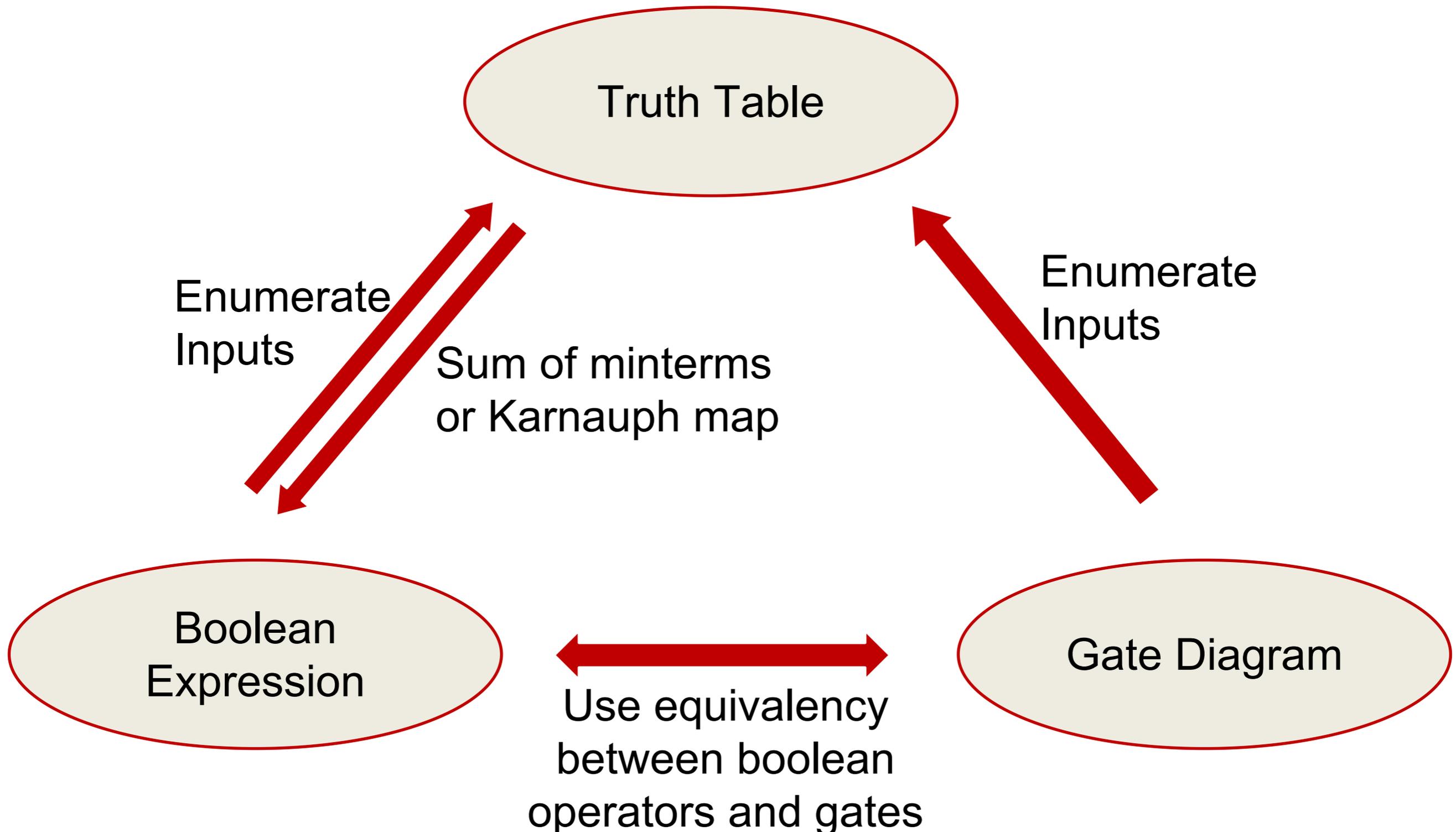


Build Larger Blocks—like LEGO®

Build a full adder (FA): truth table

$$\begin{array}{r} 01010101 \\ + \underline{01110011} \\ \hline \end{array}$$

Carry in	A	B	Sum	Carry out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

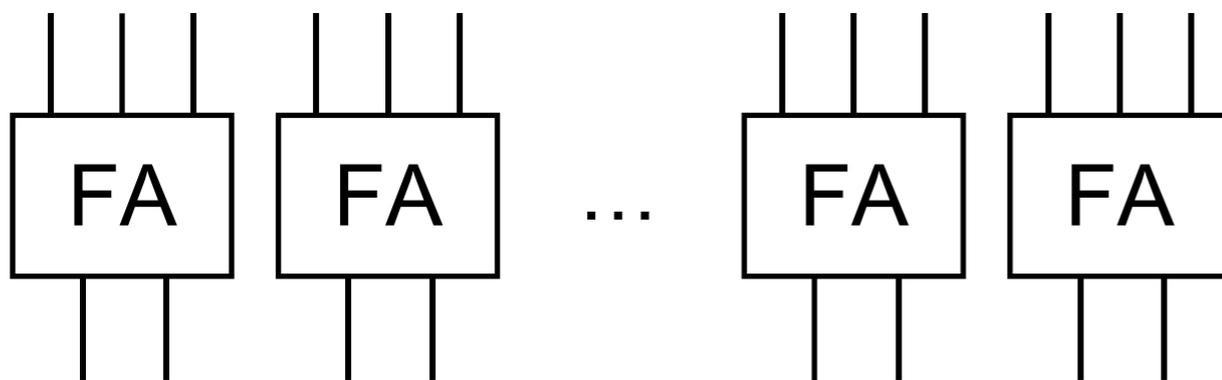

Exercise

- Recall beq instruction. Build a comparator that makes the decision. 1 indicates “equal”, 0 indicates “not equal”

Other Useful Combinational Circuits

- Multiplexer (2^n -to-1)

